

Two equal reservoirs (10x10x100cm) of salt- ($\rho=0.22 \Omega\text{m}$) and freshwater ($\rho=2.4 \cdot 10^5 \Omega\text{m}$) are put in parallel into a circuit on a battery.

- How much current flows through each of the reservoirs and how much power is put out by each one of those?

